

## Mini Project

Pranav Konduru | Jose Guerra Fajardo

### ALU

- Following test cases:

```
128 // Initialize inputs
129 a = 0;
130 b = 0;
131 cin = 0;
132 operation = 4'b0000;
133
134 // Test addition
135 #10 a = 32'd100; b = 32'd50; operation = 4'b0000; // Add a + b
136 #10 a = 32'd2147483647; b = 32'd1; operation = 4'b0000; // Test for overflow
137
138 // Test subtraction
139 #10 a = 32'd100; b = 32'd50; operation = 4'b0001; // Subtract a - b
140 #10 a = 32'd0; b = 32'd1; operation = 4'b0001; // Test for underflow
141
142 // Test multiplication
143 #10 a = 32'd200000000; b = 32'd200000000; operation = 4'b0010; // Multiply a * b
144 // #10 a = 32'd9; b = 32'd3; operation = 4'b0010; // Multiply a * b
145
146 // Test AND operation
147 #10 a = 32'hFFFF0000; b = 32'h0000FFFF; operation = 4'b0011; // AND
148
149 // Test OR operation
150 #10 a = 32'hFFFF0000; b = 32'h0000FFFF; operation = 4'b0100; // OR
151
152 // Test XOR operation
153 #10 a = 32'hAAAA5555; b = 32'h5555AAAA; operation = 4'b0101; // XOR
154
155 // Test NOT operation
156 #10 a = 32'hAAAAAAAA; operation = 4'b0110; // NOT
157
158 // Test EqualTo comparator
159 #10 a = 32'h0000000F; b = 32'h0000000F; operation = 4'b0111; // EqualTo
160
161 // Test LessThan comparator
162 #10 a = 32'h00000001; b = 32'h0000000F; operation = 4'b1000; // LessThan
163
164 // Test LessThanEqualTo comparator
165 #10 a = 32'h0000000F; b = 32'h0000000F; operation = 4'b1001; // LessThanEqualTo
166
167 #10 $finish;
168 end
```


- Inputs are signed 32 bit integers and the opcode used to select the ALU operation. Outputs are 32 bit results and flag bits for overflow, underflow, and the rest of the comparator flags

Mnemonic	Opcode (4-bit)	Description
ADD	0000	Add two registers
SUB	0001	Subtract two registers
MUL	0010	Multiply two registers
AND	0011	AND operation between registers
OR	0100	OR operation between registers
XOR	0101	XOR operation between registers
NOT	0110	NOT operation on a register
CMP_EQ (EqualTo)	0111	Compare Equal
CMP_LT (LessThan)	1000	Compare Less Than
CMP_LTE (LessThanEqualTo)	1001	Compare Less Than or Equal
LOAD	1010	Load data from memory
STORE	1011	Store data to memory
JMP	1100	Unconditional jump to register
JMP_COND	1101	Conditional jump based on CC
CALL	1110	Call a procedure (save state)
RET	1111	Return from procedure (restore state)


```

assign opcode = instruction[31:28]; // 4-bit opcode
assign reg1 = instruction[27:24]; // Source register 1
assign reg2 = instruction[23:20]; // Source register 2
assign reg_dest = instruction[19:16]; // Destination register

```

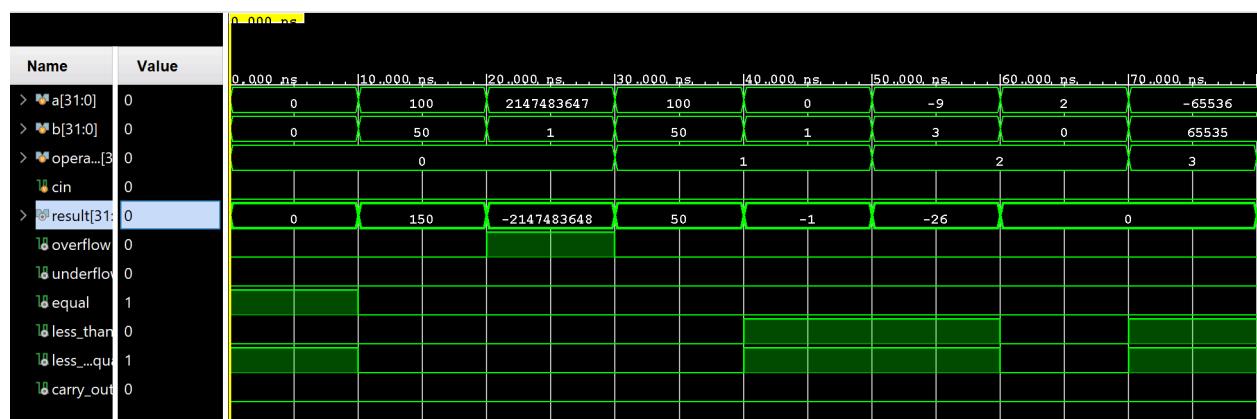

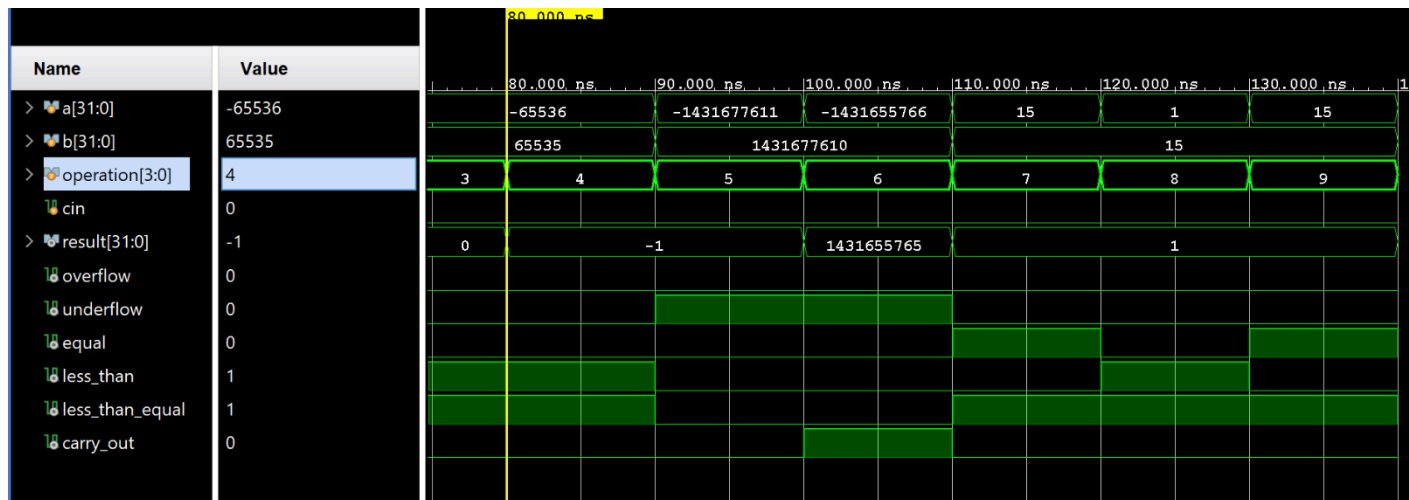Waveform that shows the results for the first four operations: ADD, SUB, MULT, AND



Waveform that shows the results for the first four operations: OR, XOR, NOT, Equal, Less Than, Less Than Equal To

## Registers

- Tested reading and writing to the 16 32-bit register files by feeding values along with the register location.
- Setup a write flag condition where data can only be written once the signal (write flag) is high
- Setup a condition for the PC and SP so that data fed to their designated address will go to their assigned register.

```

110 ○ | #10 reset = 0; // Deassert reset after 10 time units
111 |
112 | // Test writing to registers
113 ○ | #10 write_reg = 4'b0010; write_data = 32'd123; reg_write = 1; // Write 123 to R2
114 ○ | #10 write_reg = 4'b0011; write_data = 32'd456; reg_write = 1; // Write 456 to R3
115 ○ | #10 write_reg = 4'b0100; write_data = 32'd789; reg_write = 1; // Write 789 to R4
116 |
117 | // Test reading from registers
118 ○ | #10 reg_write = 0; read_reg1 = 4'b0010; read_reg2 = 4'b0011; // Read R2 and R3
119 ○ | #10 $display("Read R2 = %d, R3 = %d", reg_data1, reg_data2); // Expect 123 and 456
120 |
121 | // Test reading from R0 (PC) and R1 (SP)
122 ○ | #10 read_reg1 = 4'b0000; read_reg2 = 4'b0001; // Read PC (R0) and SP (R1)
123 ○ | #10 $display("Read PC = %d, SP = %d", reg_data1, reg_data2); // Expect PC and SP values
124 |
125 | // Test updating the Condition Code (CC) register
126 ○ | #10 cc_flags = 5'b10101; // Set some flags
127 ○ | #10 $display("CC Flags updated to: %b", cc_flags);
128 |
129 | // Test program counter increment
130 ○ | #20 $display("PC after increment: %d", pc);
131 |

```



```

45 |
46 | // Monitor values and step through different addresses to simulate instruction fetch
47 | #10 addr = 32'd0; // Fetch instruction at address 0
48 | #10 addr = 32'd1; // Fetch instruction at address 1
49 | #10 addr = 32'd2; // Fetch instruction at address 2
50 | #10 addr = 32'd3; // Fetch instruction at address 3
51 | #10 addr = 32'd4; // Fetch instruction at address 4
52 | #10 addr = 32'd5; // Fetch instruction at address 5
53 | #10 addr = 32'd6; // Fetch instruction at address 6
54 | #10 addr = 32'd7; // Fetch instruction at address 7
55 | #10 addr = 32'd8; // Fetch instruction at address 8
56 | #10 addr = 32'd9; // Fetch instruction at address 9
57 |
58 | #10 $finish; // End the simulation
59 | end
60 |
61 | // Monitor and display instruction fetch
62 | always @(addr or instruction) begin
63 |     $display("%0t ns | Address: %0d | Instruction: %b", $time, addr, instruction);
64 | end

```

Input is the memory address and the output is the instruction stored at that address

Name	Value	
> addr[31:0]	00000000	00000000
> instruction[31:0]	00000010000000110000	00000001


00000000	00000001
00000010000000110000	00010011010001010000000000000000

## Control Unit

```

69 | $display("Testing a regular operation (opcode 4'b0001)...");
70 | instruction = 32'b0001_0001_0010_0011_0000000000000000; // opcode = 4'b0001, src1=4'b0001, src2=4'b0010, dest=4'b0011
71 | #10;
72 | $display("Operation: %b, Src1: %b, Src2: %b, Dest: %b, Reg Write: %b", operation, src1, src2, dest, reg_write);
73 |
74 | // Test 2: Immediate operation
75 | $display("Testing an immediate operation (opcode 4'b0100)...");
76 | instruction = 32'b0100_0010_0011_0100_0000000000001010; // opcode = 4'b0100, src1=4'b0010, dest=4'b0100, immediate=16'b10
77 | #10;
78 | $display("Operation: %b, Src1: %b, Src2: %b, Dest: %b, Immediate: %d, Use Immediate: %b", operation, src1, src2, dest, im
79 |
80 | // Test 3: Another regular operation
81 | $display("Testing another regular operation (opcode 4'b0010)...");
82 | instruction = 32'b0010_0101_0110_0111_0000000000000000; // opcode = 4'b0010, src1=4'b0101, src2=4'b0110, dest=4'b0111
83 | #10;
84 | $display("Operation: %b, Src1: %b, Src2: %b, Dest: %b, Reg Write: %b", operation, src1, src2, dest, reg_write);
85 |
86 | // Test 4: Immediate operation with reset applied during instruction execution
87 | $display("Testing immediate operation with reset...");
88 | instruction = 32'b0100_1000_1001_1010_000000000001111; // opcode = 4'b0100, src1=4'b1000, dest=4'b1010, immediate=16'b11
89 | #5;
90 | reset = 1; // Apply reset in the middle of execution

```

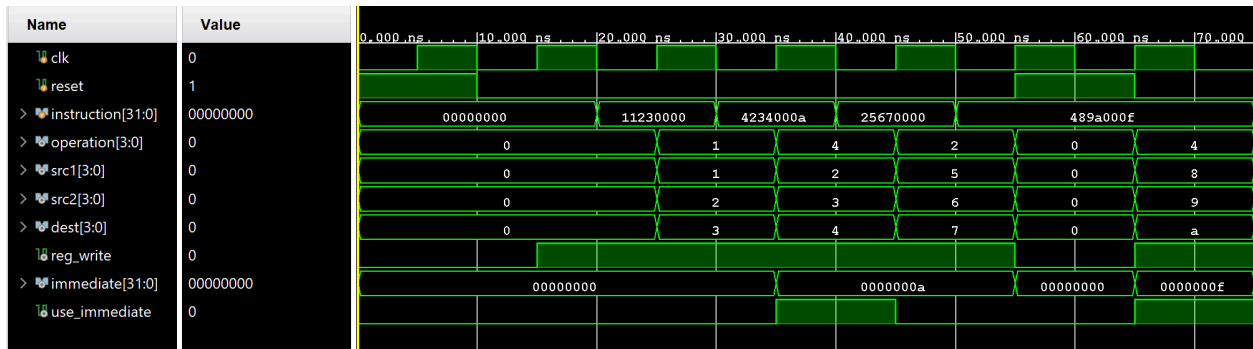


## CPU module


```

38 // Clock generation
39 always #5 clk = ~clk; // Toggle clock every 5 time units
40
41 initial begin
42     // Initialize inputs
43     clk = 0;
44     reset = 1; // Start with reset active
45
46     // Print initial state
47     $display("Starting CPU Testbench...");
48
49     // Deassert reset after 10 time units
50     #10 reset = 0;
51
52     // Run simulation for a few clock cycles
53     #100;
54
55     // Finish the simulation
56     $finish;
57 end


```

 Inputs are clock and reset signal. Output is the result getting stored in the register.



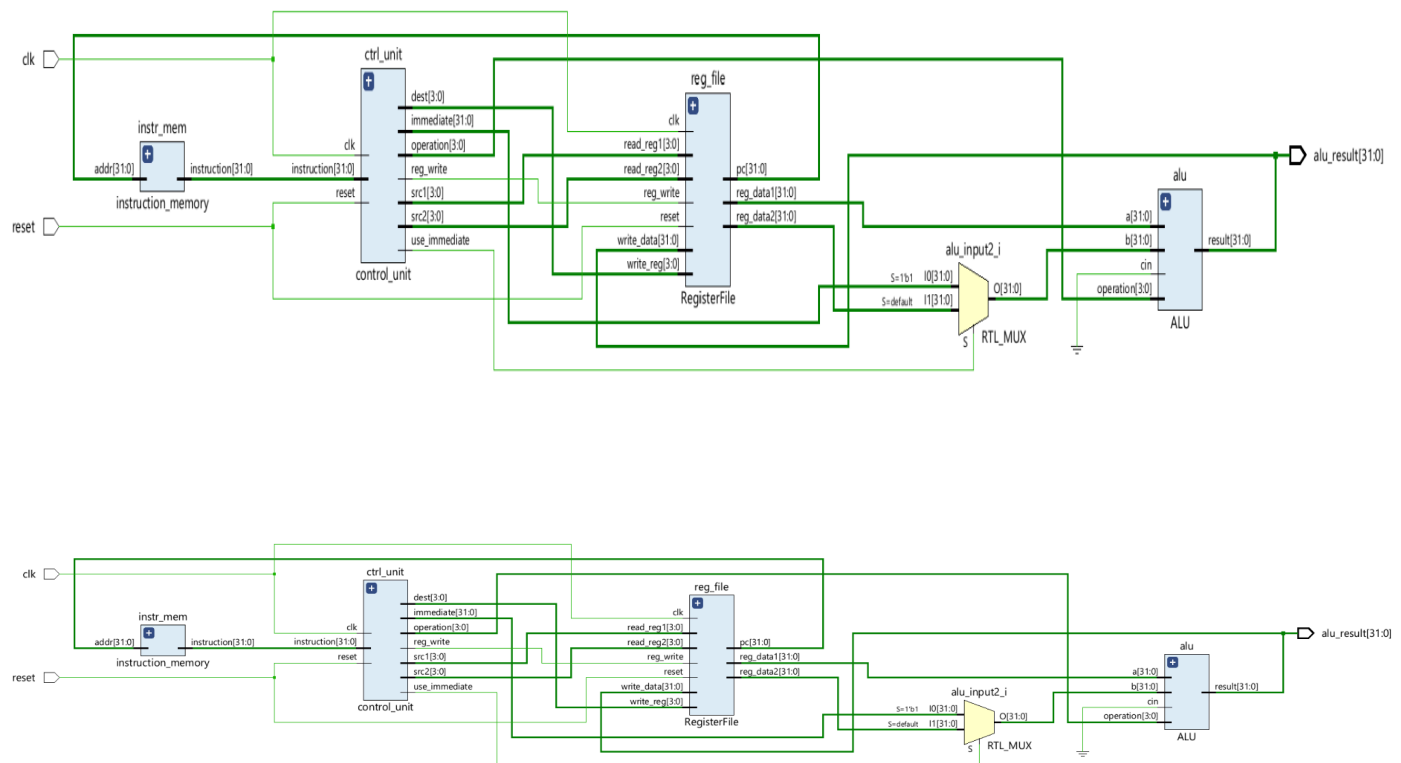

Final schematic of our design.

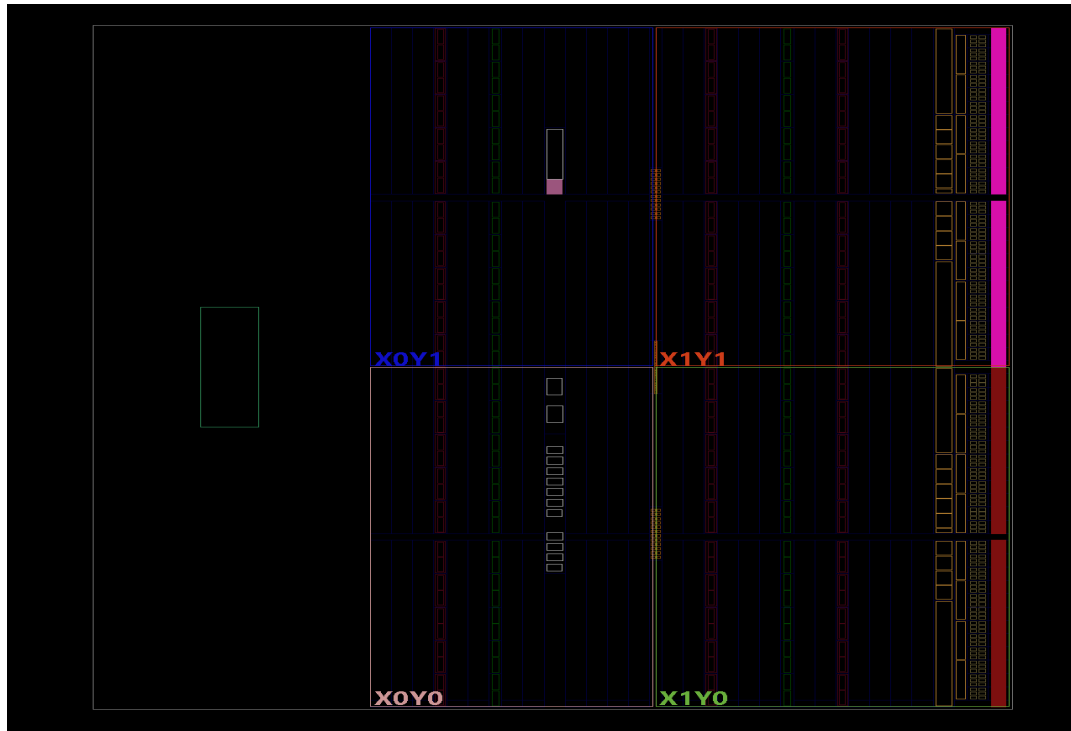

Final Device

## Conclusion

The CPU module design consists of four components: ALU, register file, instruction memory, and control unit. Each of these components were tested with their own testbench and simulated in the waveforms. The overall result, however, did not produce the expected results. Either the instructions are not reaching the control unit correctly or the register file is not updating due to not recognizing the instructions. (We will follow up with these problems and debug them) Although the project does not operate correctly in the end, it helped us understand how instructions are generally passed in a RISC based computer architecture system.